
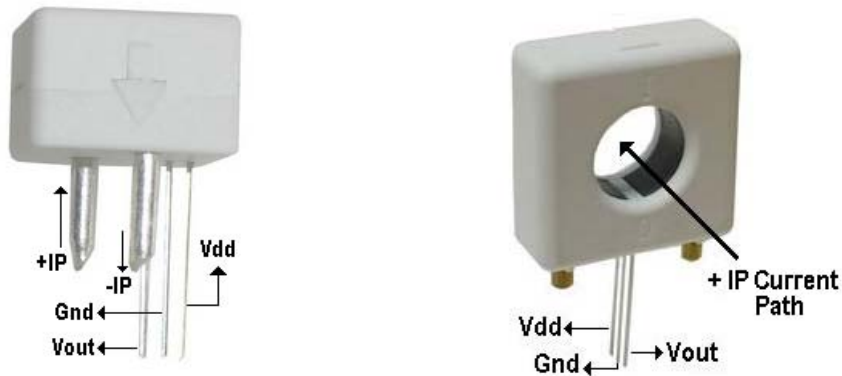


WCS current sensor Application note

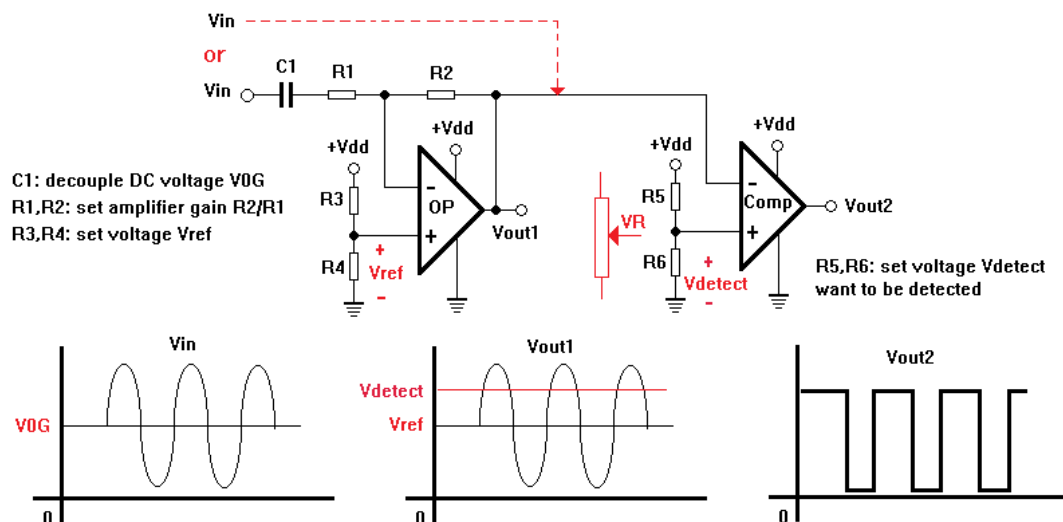

To precisely measure the current by using WCS series products is easy and straight forward. First connect the conductor in series with the current path you plan to measure (or pass conductor through the conductor hole) and apply 5V between Vdd and Gnd (Fig. above). Then you already finish the hardware settlement of WCS series current sensor.



Over current detection:



The above circuit can detect current and protect your system from over current or short circuit.

DC Current measurement:

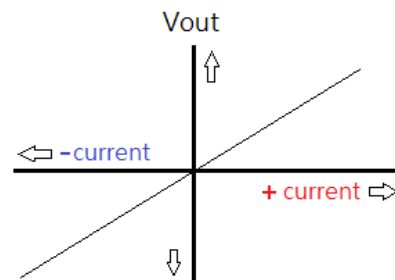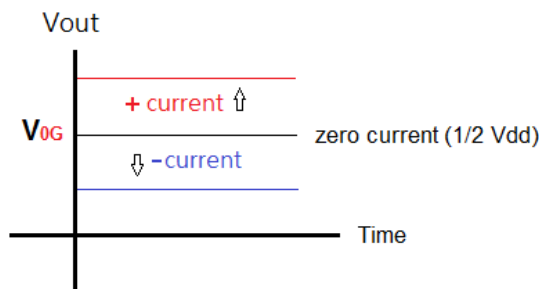1. **Zero current:** measure the output's voltage V_{0G} when no current pass through.
2. **Calibration:** Pass an already known current (for example: 10A) through the current sensor and measure the output voltage V_{10A} . The sensitivity of this current sensor is **Sensitivity = $(V_{10A} - V_{0G})/10A$ unit: V/A**
3. **Start Measurement:** you can measure any current by the following equation. **Current = $(V_{out} - V_{0G})/\text{Sensitivity}$ (A)**






AC Average Current measurement:

1. **Zero current:** measure the output's voltage V_{0G} when no current through.
2. **Software Solution:**
 - 2.1 Pass an already known AC current (for example: 10A) through the current sensor
 - 2.2 Connect sensor's output signal V_{out10A} directly into analog input of micro-controller
 - 2.3 Write a program to calculate the area of several TT periods of AC signal, the higher sampling rate per TT period the more precision you get.
 - 2.4 Divide "Area/TT" and get the average value of V_{out10A}

$$V_{out10A \text{ average}} = \text{Average}(\sum |V_{out} - V_{0G}|)$$
 - 2.5 Calibrate the Sensitivity of current sensor by
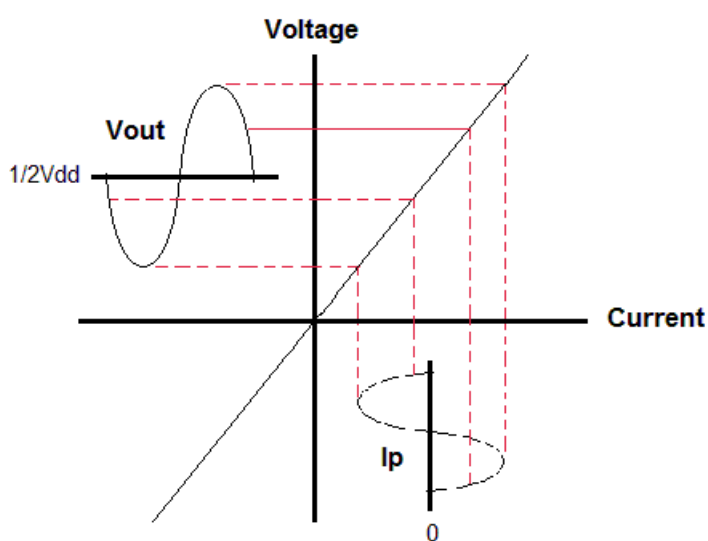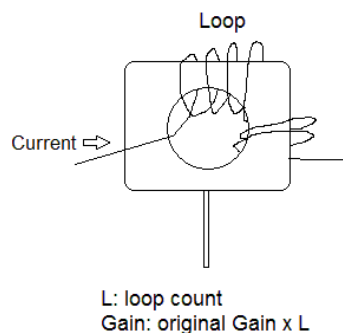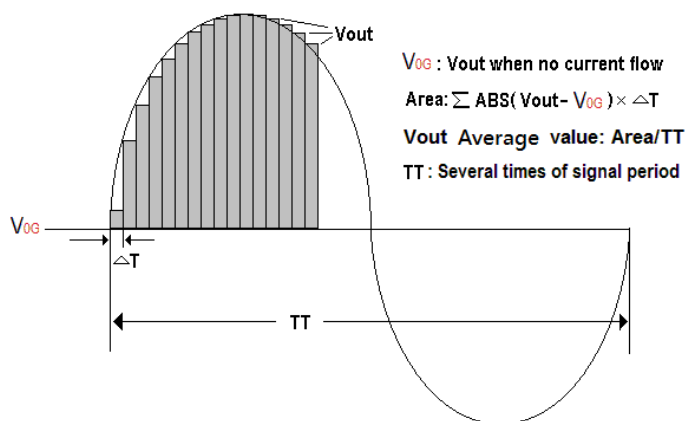
$$\text{Sensitivity} = V_{out10A \text{ average}} / 10 \text{ unit: V/A}$$
 - 2.6 Start Measurement: Use the same program to measure any current by equation **Current = $V_{out}/\text{sensitivity}$ (A)**



3. Hardware Solution:

3.1 Pass an already known AC current (for example: 10A) through the current sensor

3.2 Connect sensor's output signal V_{out10A} into AC amplifier circuit listed below to remove DC part V_{0G} and amplify it, **Amplify Gain = $R2/R1$**

3.3 Procure the average value of V_{out10A} and calculate sensitivity

Sensitivity = $V_{out10A}/10$ unit: V/A

3.4 Start Measurement: measure any current by the following equation

Current = $V_{out}/\text{sensitivity}$ (A)

